

Topic 3


Kirchhoff's laws:

Kirchhoff's Voltage Law (KVL),

Kirchhoff's Current Law (KCL)

Kirchhoff's Voltage Law (Mesh Law)

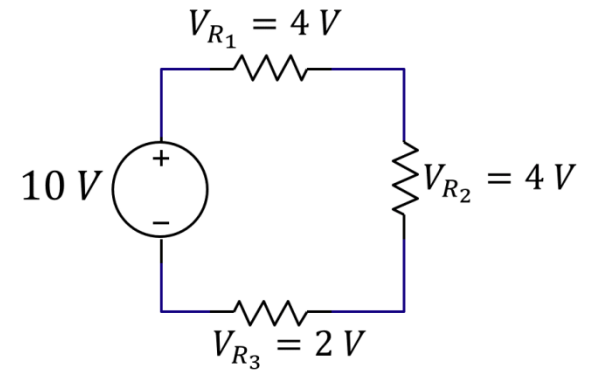
Around any complete (closed loop) circuit, the algebraic sum of the electromotive force equals the algebraic sum of the voltage drops.



$$\sum \text{Voltage}_{rise} = \sum \text{Voltage}_{drop}$$

$$10V = 4V + 4V + 2V$$

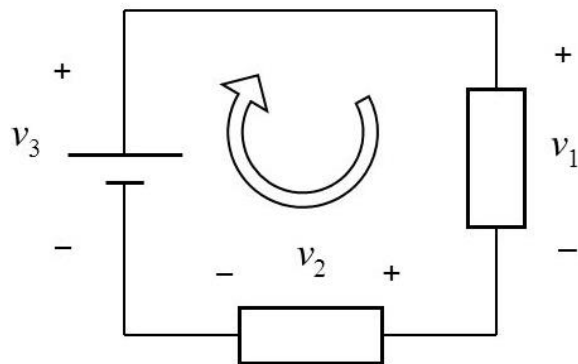“The algebraic sum of all voltages around any closed path in a circuit is zero” (positive for a voltage rise, negative for a voltage drop).



$$+v_1 + v_2 - v_3 = 0$$

$$-v_1 - v_2 + v_3 = 0$$


$$v_1 + v_2 = v_3$$

Example:

According to KVL,


$$10V - 8V - 6V = 2I + 3I + 5I + 7I$$
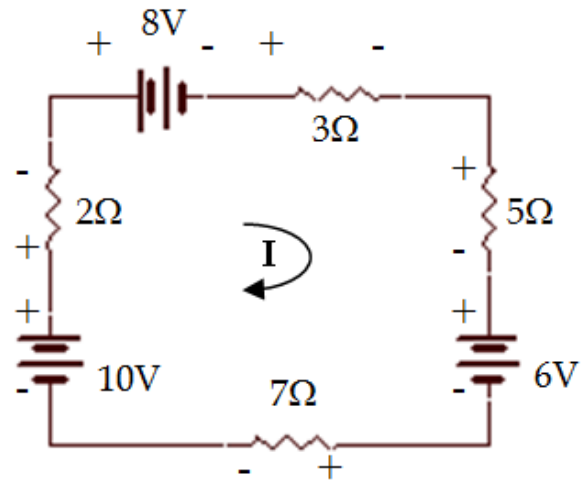
$$\text{Or, } 8V + 6V - 10V + 2I + 3I + 5I + 7I = 0$$



Kirchhoff's Current Law (Point Law)

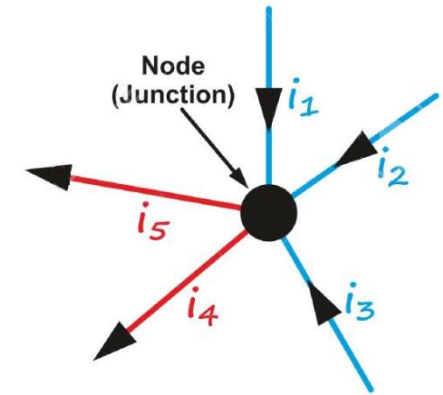In any electrical network, the algebraic sum of the currents meeting at a point or junction is zero. i.e $\sum I$ (incoming current) = $\sum I$ (leaving current).



$$I_1 + I_2 + I_3 = I_4 + I_5$$


or, $\sum I_{\text{enter}} = \sum I_{\text{leave}}$

or, $\sum I_{\text{enter}} - \sum I_{\text{leave}} = 0$

The algebraic sum of the currents entering and leaving a node is equal to zero


$$\sum I = 0$$

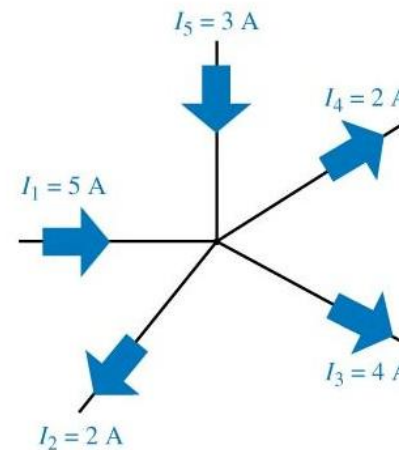Currents entering a node are positive and those leaving a node are negative.



$$\sum_{n=1}^N I_n = I_1 + (-I_2) + (-I_3) + (-I_4) + I_5 = 0$$

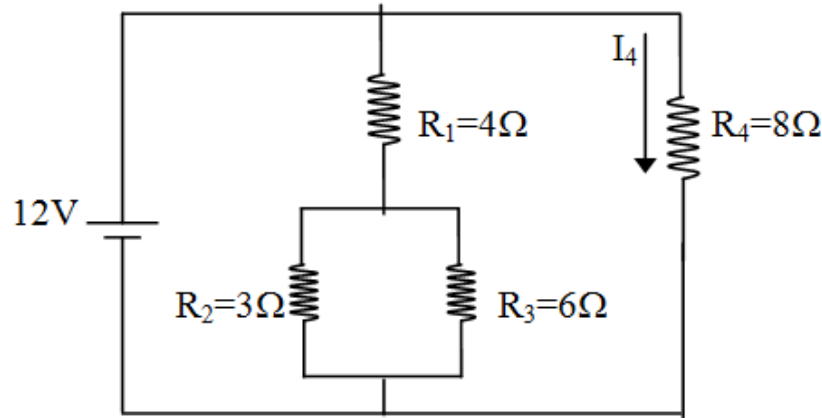Problem-1) Determine the current I_4 & the voltage V_2 for the network of the figure



Solution:

$$R_T = \{R_1 + (R_2 \parallel R_3)\} \parallel R_4 = \{4 + (3 \parallel 6)\} \parallel 8 = (4 + 2) \parallel 8 = 6 \parallel 8 = 3.43 \Omega$$

$$I = \frac{E}{R_T} = \frac{12}{3.43} = 3.50A$$

$$I_4 = \frac{I \times R_{123}}{R_{123} + R_4} = \frac{3.5 \times 6}{6 + 8} = 1.5A$$

Again, $I_1 = 2A$ through R_1 resistor. So,

$$I_2 = \frac{I_1 \times R_3}{R_2 + R_3} = \frac{2 \times 6}{3 + 6} = \frac{12}{9} = 1.33A$$

$$\therefore V_2 = I_2 \times R_2 = 1.33 \times 3 = 4V$$

Alternative solution:

$$I_4 = \frac{E}{R_4} = \frac{12}{8} = 1.5A$$

Alternative solution:

$$R_{23} = R_2 \parallel R_3 = 3 \parallel 6 = 2\Omega$$

Applying voltage divider rule

$$V_2 = \frac{R_{23} \times E}{R_1 + R_{23}} = \frac{2 \times 12}{4 + 2} = 4V$$

Problem-2) Find the values of V_1 , V_3 , V_{ab} & I_s for the network.

